

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/MANAGEMENT/
COMMERCIAL PRACTICE, NOVEMBER - 2022**

INDUSTRIAL ELECTRONICS AND CONTROL DRIVES

[Maximum marks: 100]

(Time: 3 Hours)

PART – A

Maximum marks : 10

I (Answer *all* the questions in one or two sentences. Each question carries 2 marks)

1. Define the term holding current.
2. What is an inverter?
3. Write Fleming's left hand rule.
4. List the applications of servomotor.
5. What is a chopper?

(5 x 2 = 10)

PART – B

Maximum marks : 30

II (Answer any *five* of the following questions. Each question carries 6 marks)

1. With figures briefly explain transistor analogy of SCR.
2. Describe the constructional features of SCR.
3. Describe the working of Triac light dimming circuit.
4. Briefly describe Class A commutation.
5. Explain the principle of operation of Universal motor.
6. With a neat sketch briefly explain the working principle of DC tachogenerator.
7. Briefly explain about AC Chopper.

(5 x 6 = 30)

PART – C

Maximum marks : 60

(Answer one full question from each unit. Each full question carries 15 marks)

UNIT –I

III.(a) Explain the role of snubber circuit.

(8)

(b) Describe RC triggering of SCR. (7)

OR

IV.(a) Explain the working of Triac and draw its VI characteristics. (8)

(b) Describe R triggering of SCR. (7)

UNIT-II

V. (a) Explain single phase half wave bridge inverter. (8)

(b) Describe the working of class E commutation. (7)

OR

VI.(a) Explain series inverter with a neat circuit diagram. (8)

(b) Explain in brief about static transfer switch. (7)

UNIT-III

VII.(a) Explain briefly the working of DC servomotor. (8)

(b) Explain the classification of DC motors. (7)

OR

VIII.(a) Explain the principle of operation of stepper motor. (8)

(b) Describe briefly the working principle of a three phase induction motor. (7)

UNIT-IV

IX. (a) Compare AC and DC drives. (8)

(b) Explain the working of step up chopper. (7)

OR

X. (a) List the applications of chopper and cycloconverter. (8)

(b) Describe the speed control method of DC drive. (7)
